

# First Order Low and High Pass Passive Filters

Greg Reynolds

27th July 2008

## First Order Low Pass Filter

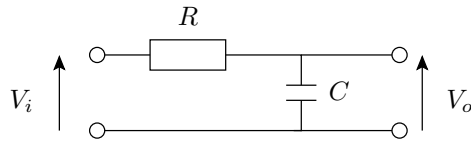


Figure 1: First order low pass filter. The current  $I_1$  flows through the resistor and capacitor, oriented in the clockwise direction.

The equations of the circuit and transfer function are:

$$V_i - I_1 R - I_1 X_C = 0 \quad (1)$$

$$I_1 X_C = V_o \quad \therefore \quad (2)$$

$$I_1 = \frac{V_o}{X_C} \quad \therefore \quad (3)$$

$$V_i - \frac{V_o}{X_C} R - \frac{V_o}{X_C} X_C = 0 \quad \therefore \quad (4)$$

$$V_i - V_o \frac{(R - X_C)}{X_C} = 0 \quad \therefore \quad (5)$$

$$\frac{V_o}{V_i} = \frac{X_C}{R - X_C} \quad (6)$$

For the  $s$ -domain description, recall that:

$$X_C = \frac{1}{sC} \quad (7)$$

which can be substituted into (6):

$$\frac{V_o}{V_i} = \frac{X_C}{R - X_C} \quad (8)$$

$$= \frac{1}{sC(R - \frac{1}{sC})} \quad (9)$$

$$= \frac{1}{sCR - 1} \quad (10)$$

To obtain the frequency response we need the magnitude of the transfer function at  $s = j\omega$ ,

$$\frac{V_o}{V_i} = \frac{1}{-1 + j\omega CR} \quad (11)$$

$$= \frac{-1 - j\omega CR}{(-1)^2 + (\omega CR)^2} \quad (12)$$

$$= \frac{-1}{1 + \omega^2 C^2 R^2} - \frac{j\omega CR}{1 + \omega^2 C^2 R^2} \quad (13)$$

the magnitude of this is obtained as follows,

$$\left| \frac{V_o}{V_i} \right|^2 = \left( \frac{-1}{1 + \omega^2 C^2 R^2} \right)^2 + \left( \frac{\omega CR}{1 + \omega^2 C^2 R^2} \right)^2 \quad (14)$$

$$= \frac{1 + \omega^2 C^2 R^2}{(1 + \omega^2 C^2 R^2)^2} \quad (15)$$

$$= \frac{1}{1 + \omega^2 C^2 R^2} \quad (16)$$

finally, taking the square root,

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}. \quad (17)$$

## First Order High Pass Filter

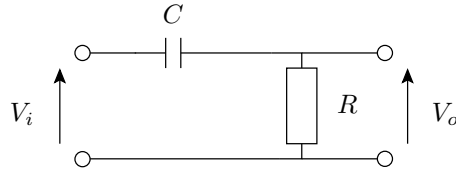


Figure 2: First order high pass filter. The current  $I_1$  flows through the capacitor and resistor, oriented in the clockwise direction.

The equations of the circuit and transfer function are:

$$V_i - I_1 X_C - I_1 R = 0 \quad (18)$$

$$I_1 R = V_o \quad \therefore \quad (19)$$

$$I_1 = \frac{V_o}{R} \quad \therefore \quad (20)$$

$$V_i - \frac{V_o}{R}(X_C + R) = 0 \quad \therefore \quad (21)$$

$$V_i = \frac{V_o}{R}(X_C + R) \quad \therefore \quad (22)$$

$$\frac{V_o}{V_i} = \frac{R}{X_C + R} \quad (23)$$

For the  $s$ -domain description, recall that:

$$X_C = \frac{1}{sC} \quad (24)$$

which can be substituted into (23):

$$\frac{V_o}{V_i} = \frac{R}{X_C + R} \quad (25)$$

$$= \frac{R}{\frac{1}{sC} + R} \quad (26)$$

$$= \frac{sCR}{1 + sCR} \quad (27)$$

To obtain the frequency response we need the magnitude of the transfer function at  $s = j\omega$ ,

$$\frac{V_o}{V_i} = \frac{j\omega CR}{1 + j\omega CR} \quad (28)$$

$$= \frac{j\omega CR(1 - j\omega CR)}{1^2 + \omega^2 C^2 R^2} \quad (29)$$

$$= \frac{j\omega CR + \omega^2 C^2 R^2}{1 + \omega^2 C^2 R^2} \quad (30)$$

$$= \frac{\omega^2 C^2 R^2}{1 + \omega^2 C^2 R^2} + j \frac{\omega CR}{1 + \omega^2 C^2 R^2} \quad (31)$$

the magnitude of this is obtained as follows,

$$\left| \frac{V_o}{V_i} \right|^2 = \frac{(\omega^2 C^2 R^2)^2 + (\omega CR)^2}{(1 + \omega^2 C^2 R^2)^2} \quad (32)$$

$$= \frac{(\omega CR)^4 + (\omega CR)^2}{(1 + \omega^2 C^2 R^2)^2} \quad (33)$$

$$= \frac{(\omega CR)^2(1 + (\omega CR)^2)}{(1 + \omega^2 C^2 R^2)^2} \quad (34)$$

$$= \frac{(\omega CR)^2}{(1 + \omega^2 C^2 R^2)} \quad (35)$$

finally, taking the square root,

$$\left| \frac{V_o}{V_i} \right| = \frac{\omega CR}{\sqrt{1 + \omega^2 C^2 R^2}}. \quad (36)$$